

Find V_x

Instant of closing switch S_1

$$V_x = V_{cc} - \text{drop across } 8k$$

$$\text{drop across } 8k = 8k \times I$$

$$I = \frac{V_{cc}}{8k + (8k \parallel 4k + 4k)}$$

$$= \frac{12}{8k + 4k} = 0.001 \text{ A} = 1 \text{ mA}$$

$$\therefore \text{drop across } 8k = 8k \times 1 \text{ mA} = 8 \text{ V}$$

Date: _____

at the instant closing the switch S_1

$$V_x = V_{cc} - 8V = 4V //$$


- steady state after closing the switch. still

$$V_x = V_{cc} - 8V = 4V //$$

- Instant of opening the switch S_1


$$V_x = 0 \quad \leftarrow \text{No storing. or storage elements.}$$

Exercise 1.1

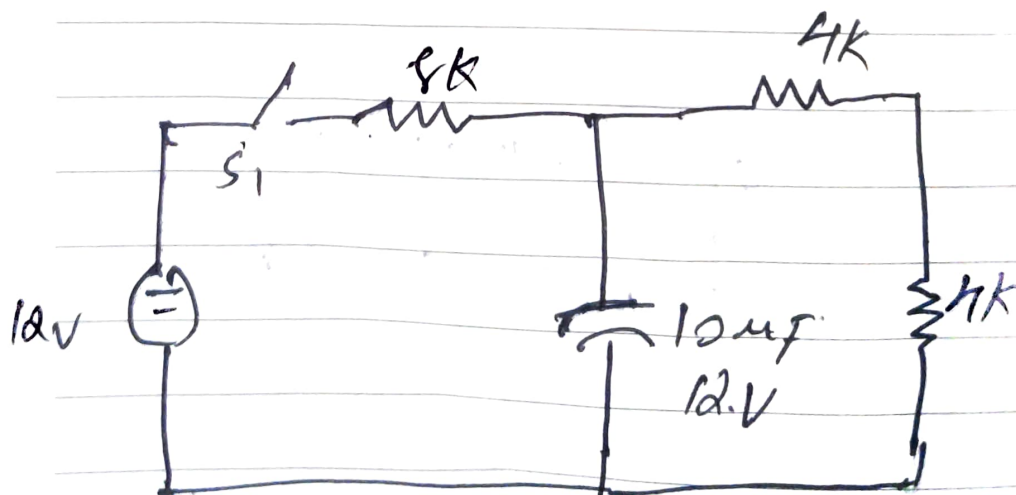


Find V_x

Instant of closing the switch.

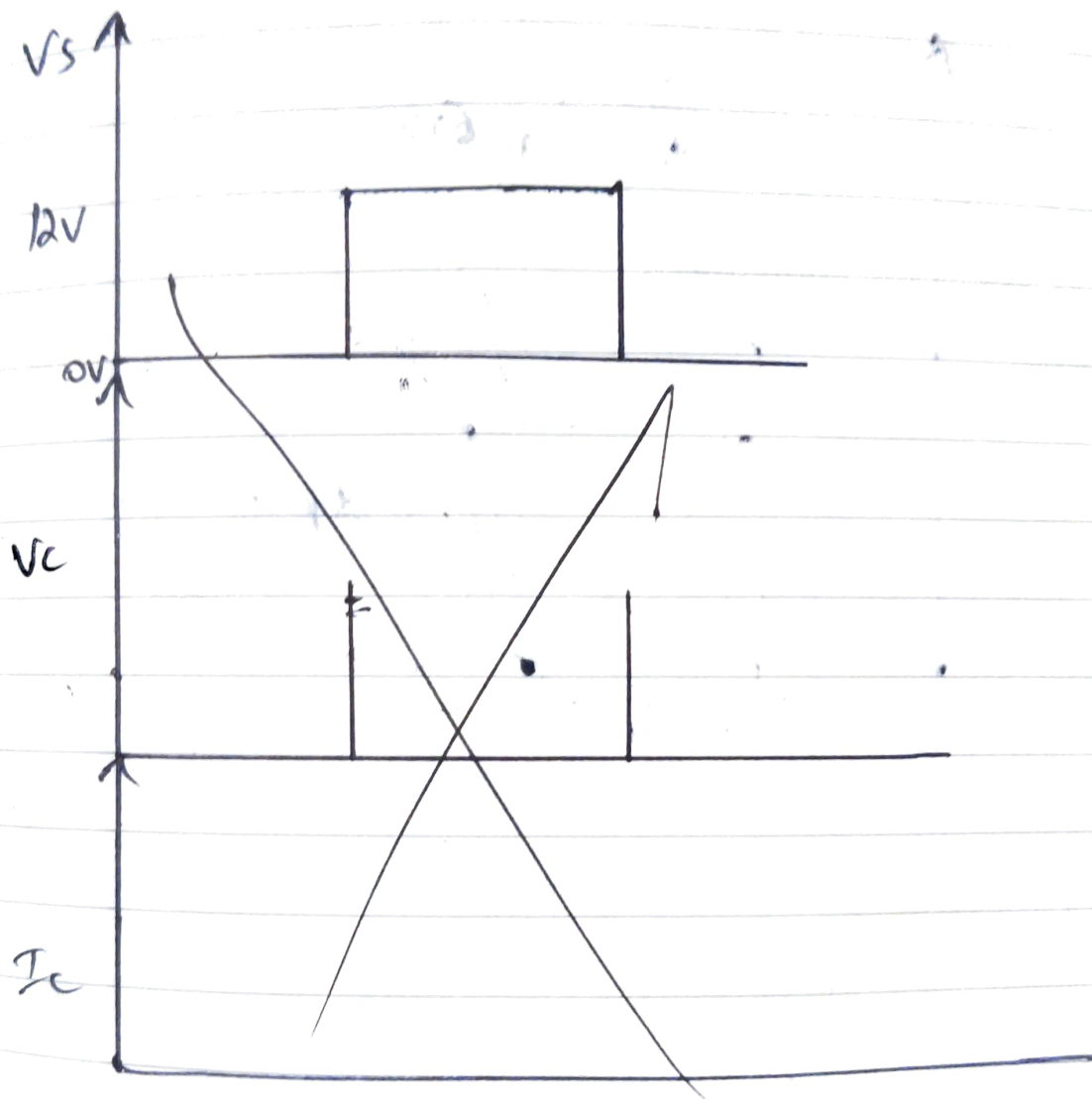


Date: _____

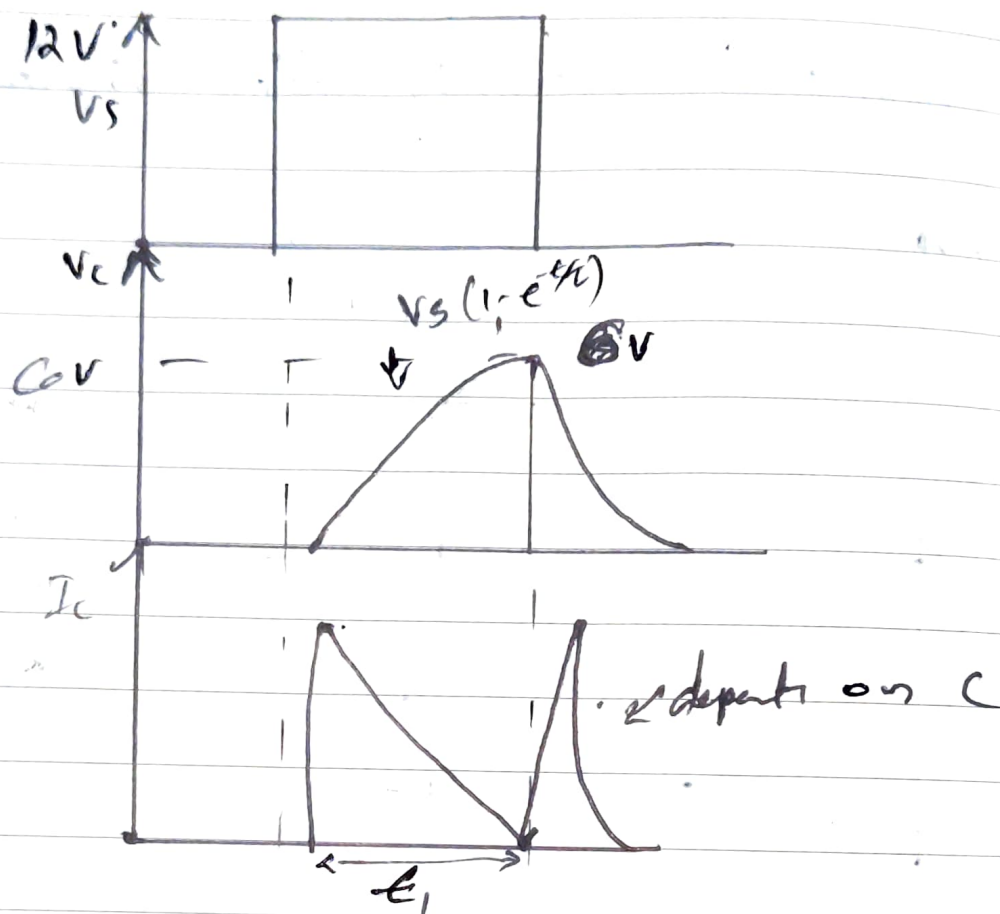

$I_c =$ maximum at start

$$= \frac{V_s}{8k}$$

$$= 1.5 \text{ mA} \Rightarrow$$

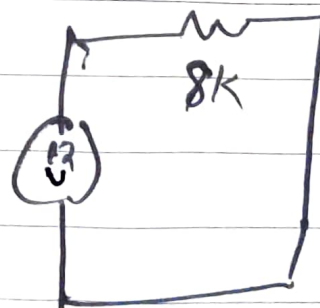


when ~~$V_c = 0$~~ \Rightarrow when $V_c = V_{c \text{ max.}}$

Date:



$$\Rightarrow 750 \mu A.$$


∴ Voltage drop $\Rightarrow V_{Cmax} =$

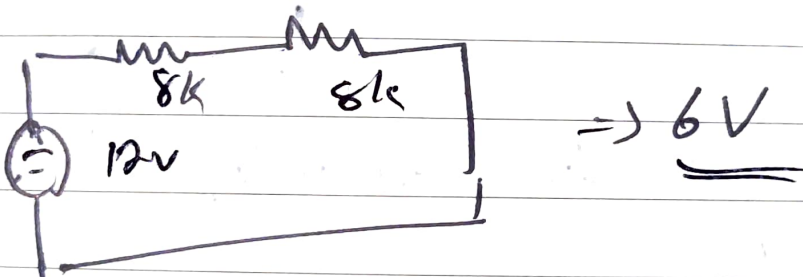

$$V_C = 6V$$

When switch is closed.


$$V_C = 6V \rightarrow 0V \dots$$

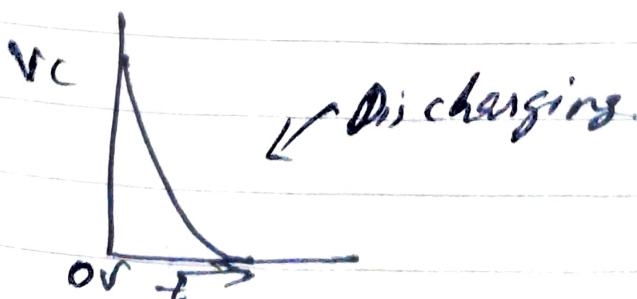


Date: _____

$$\text{Ans } I_c = \frac{V_c}{8k}$$

$$= \frac{6V}{8k} = 7.5 \times 10^{-4}$$

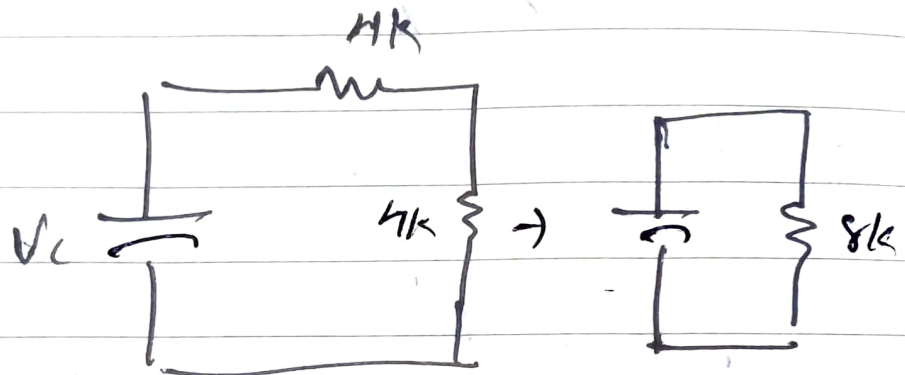

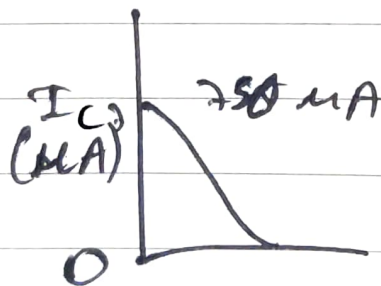which will keep reducing due to capacitor charge.



∴

• Instance of closing S_1

$$V_x = 0V$$

• Steady state after closing the switch



$$V_c = 6V \mid t \rightarrow t_s$$

Date: _____


Instant of opening the switch

$$V_C = 6V$$

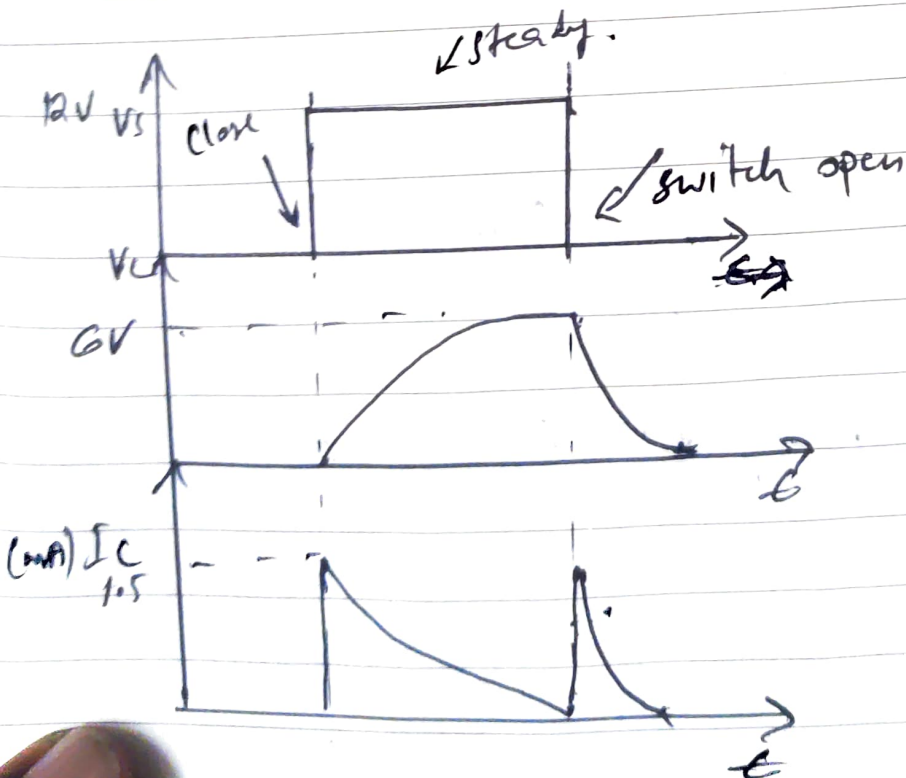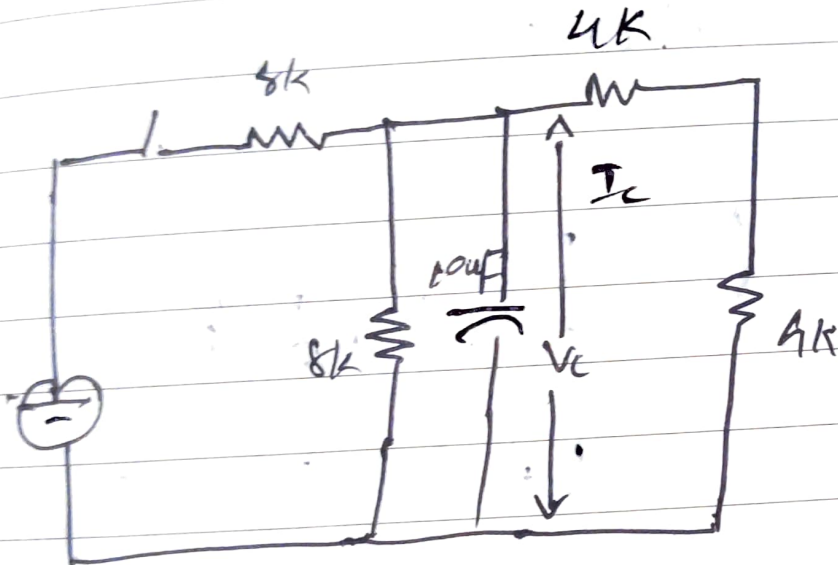
Exercise 1.21 If a switch is added in the capacitor



Date: _____

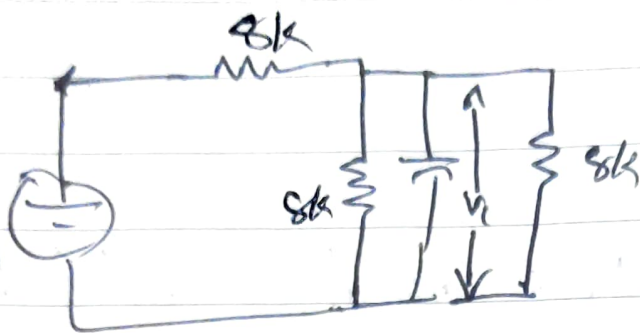

- When the switch is closed.



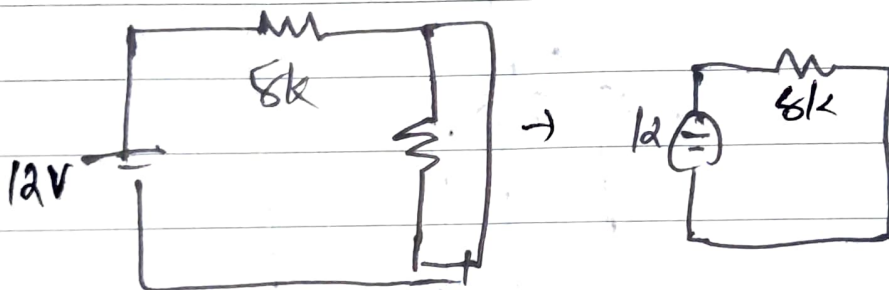


$$V_c = 0V$$

$$I_c = \frac{12}{8k} = 1.5 \text{ mA}$$

- When steady state has reached


Date: _____

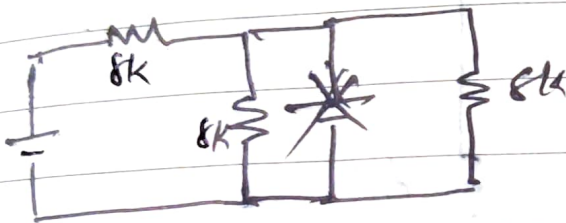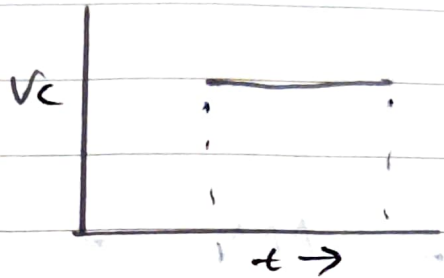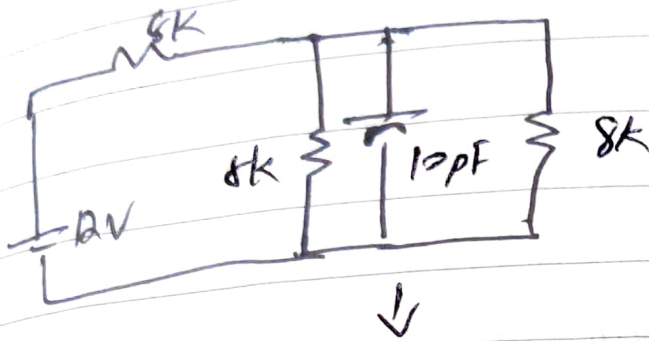


↓

$$V_C = 6\text{ V}$$

• When switch is opened.

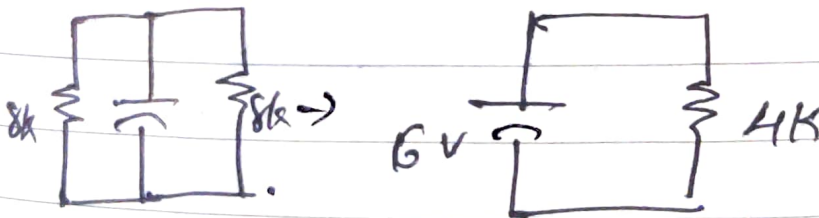



$$I_C = 1.5\text{ mA}$$

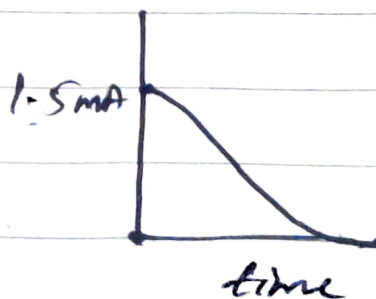

Date: _____

~~Exercice~~

Exercice 1.3

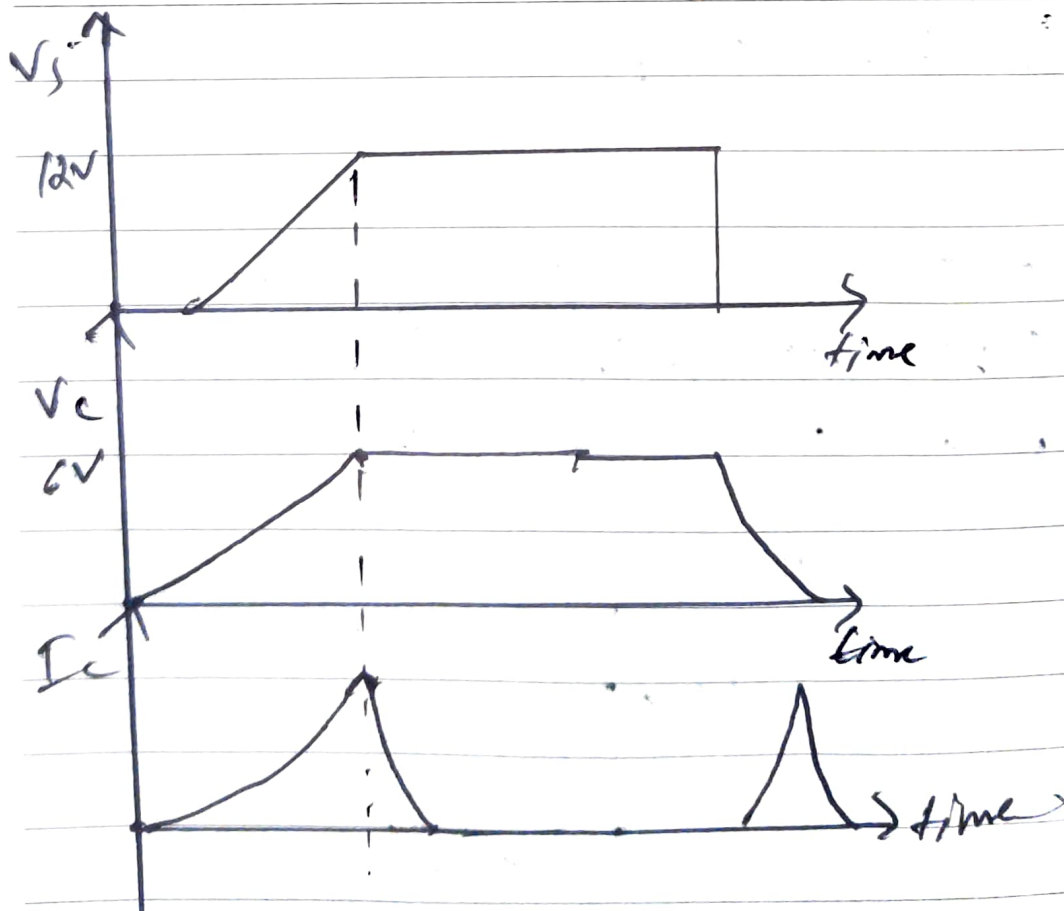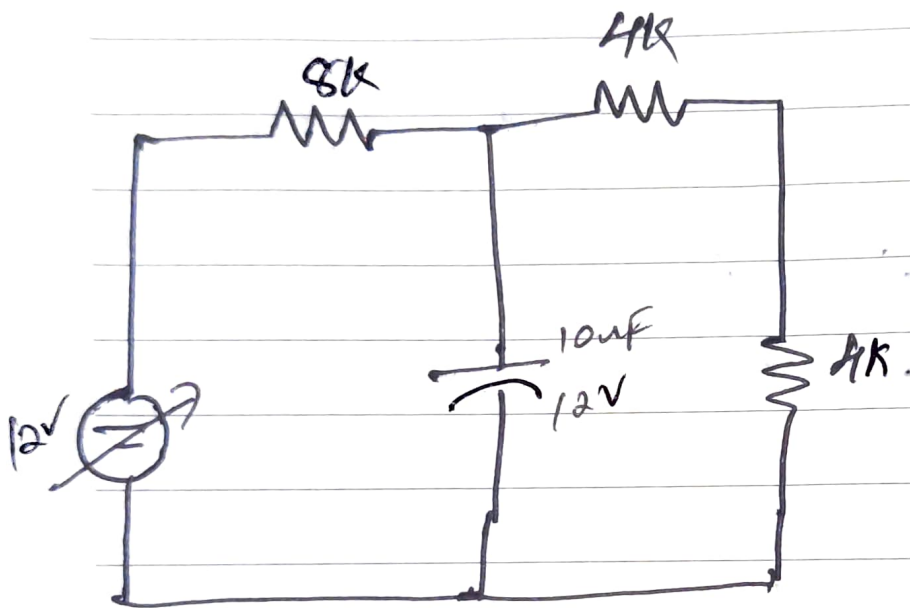



Date: _____

• when turned on $V_C = \infty$


• steady state. $V_C = 6V$

• when turned off $V_C = 6V$


Exercise 1.4

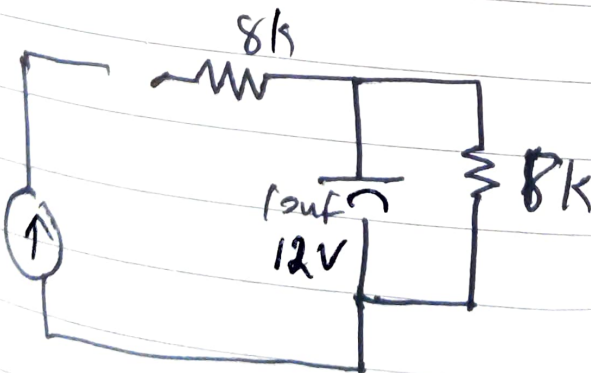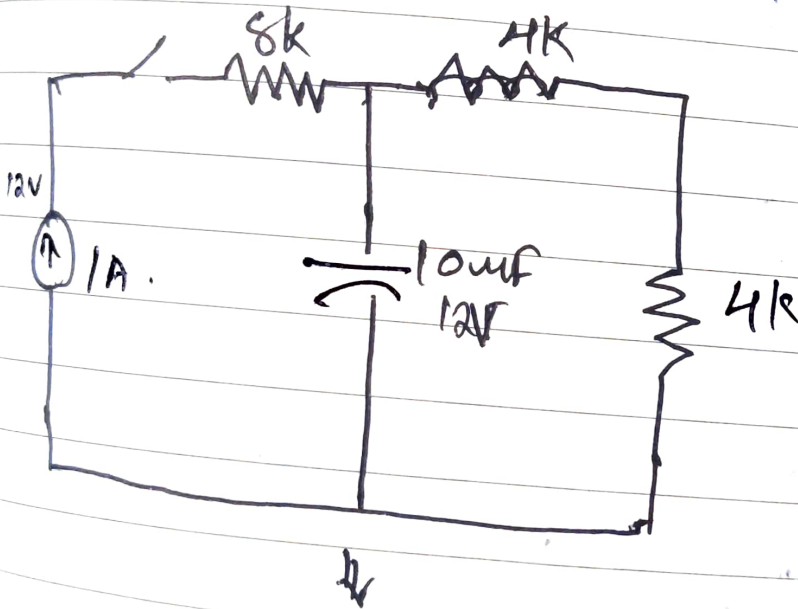

Date: _____

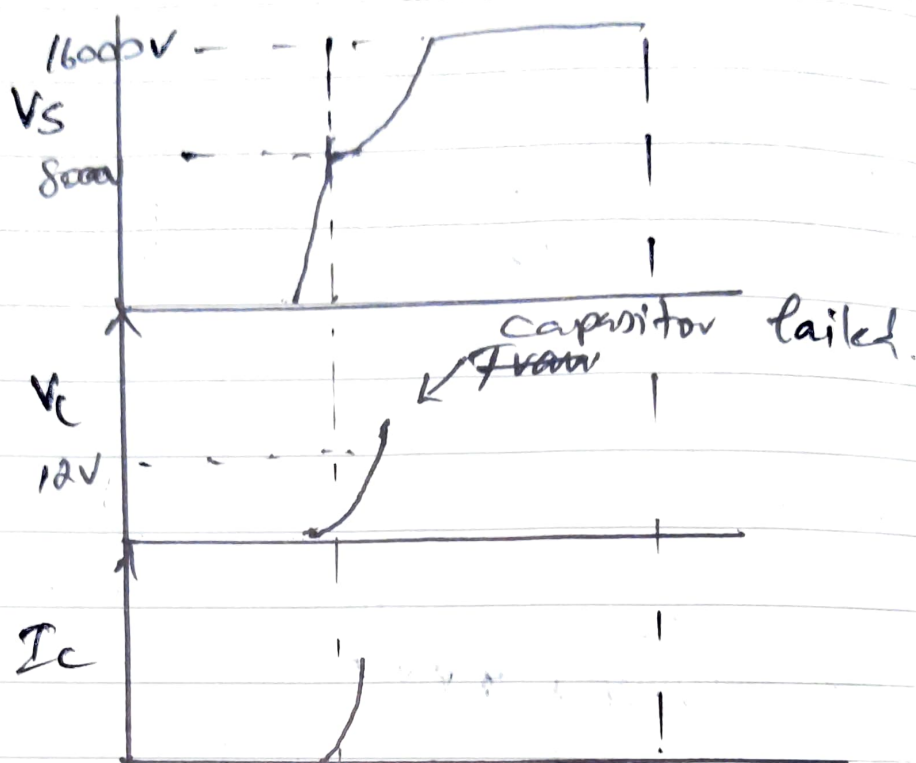

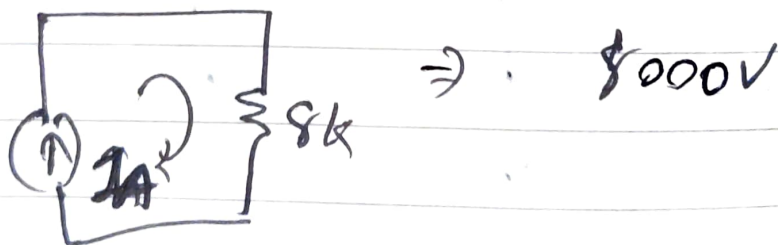• A switch close. ($C_1 = \text{close}$)
 $I_S = 1A$



$$V_S = 8000V //$$


• Steady state

$$V_C = V_{C \text{ max}} (12V)$$

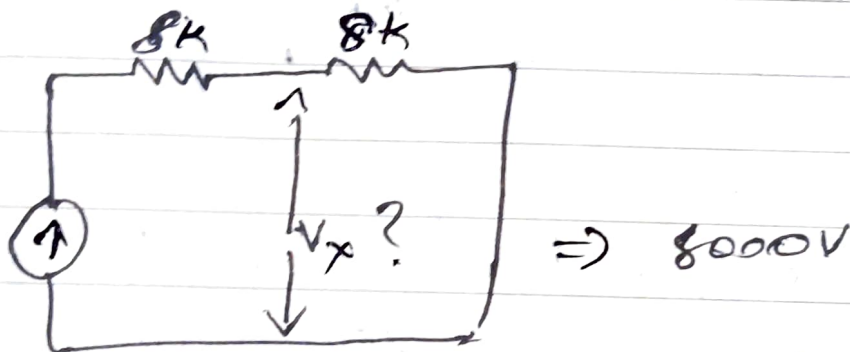Q2

the maximum value possible maximum value of $V_C = 12V$. But

there will be $8000V$ across the V_C which will break the Capacitor. either short circuit or open



$$V_S = 16000V$$

$$V_{R1} = 8000V$$


$$V_x = 8000V \quad ?$$

$$V_C \Rightarrow ? \text{ failed.}$$

$$I_C = 0A //$$

Date: _____

Exercise 2-1

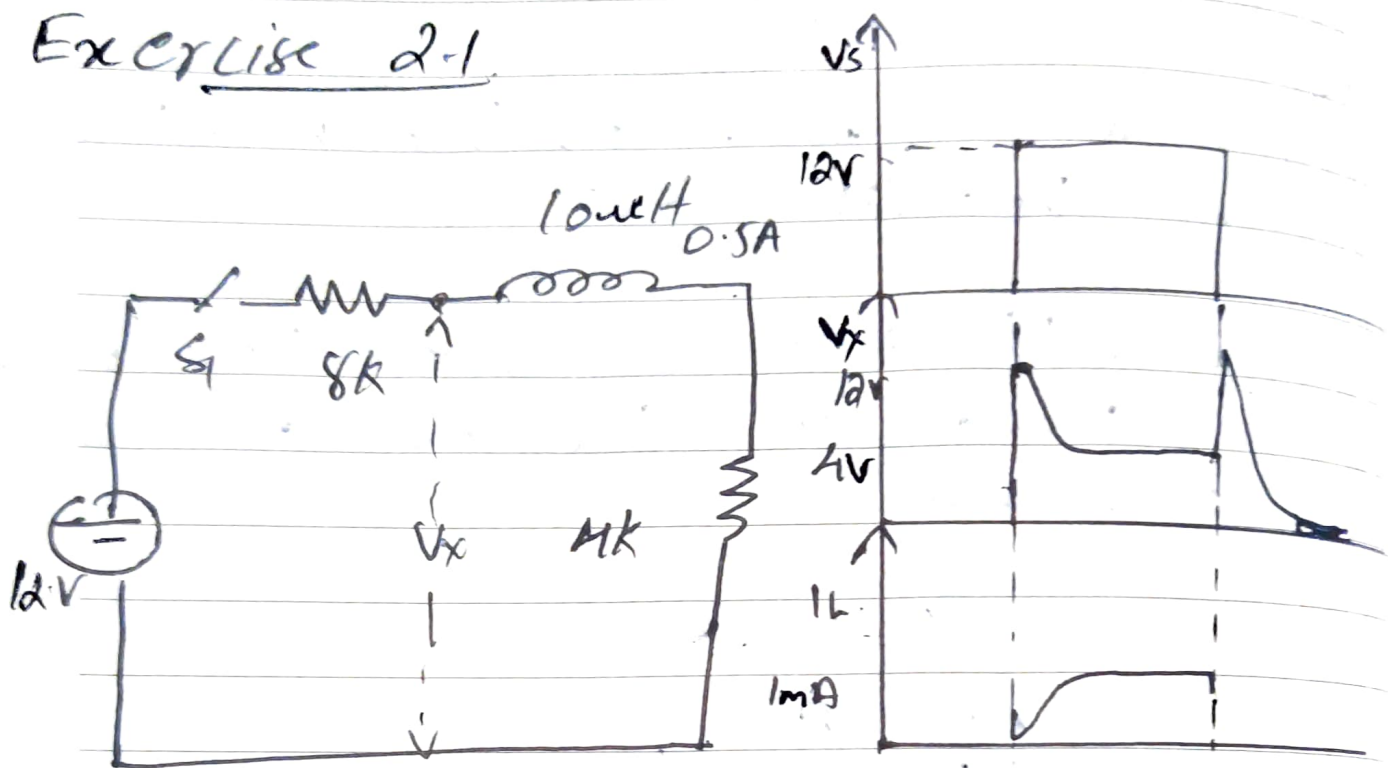

Find V_x @


- Instant of closing the switch. S_1
The inductor will resist the sudden change in current so ~~it acts as~~ at the instant it will act as open circuit then short circuit

i.e.,

$$V_x = V_s$$

$I_L = 0 \leftarrow$ Current through the inductor.

- Steady state

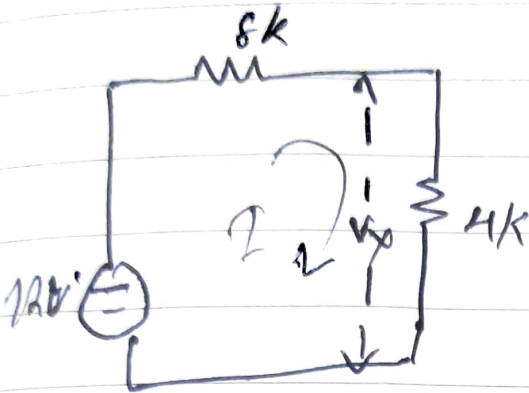

$$I = \frac{12V}{12k} = 1mA$$

$$V_x = V_s - 8k \times 1mA$$

$$= 4k \times 1mA$$

$$= 4V //$$

When switch closes the inductor will try to oppose those sudden change in current & produces an emf

But there is no path to discharge the current. therefore ~~over~~ Voltage will get multiplied by a constant (DC booster concept)

$$W = \frac{1}{2} L I^2 \Rightarrow \frac{1}{2} \times 10mH \times 0.001^2$$


$$= \frac{1}{2} \times 10 \times 10^{-6} \times 10^{-6}$$

Date: _____

$$= \underline{\underline{\frac{1}{2} \times 10^{-12}}}$$


=

Exercise 2.2

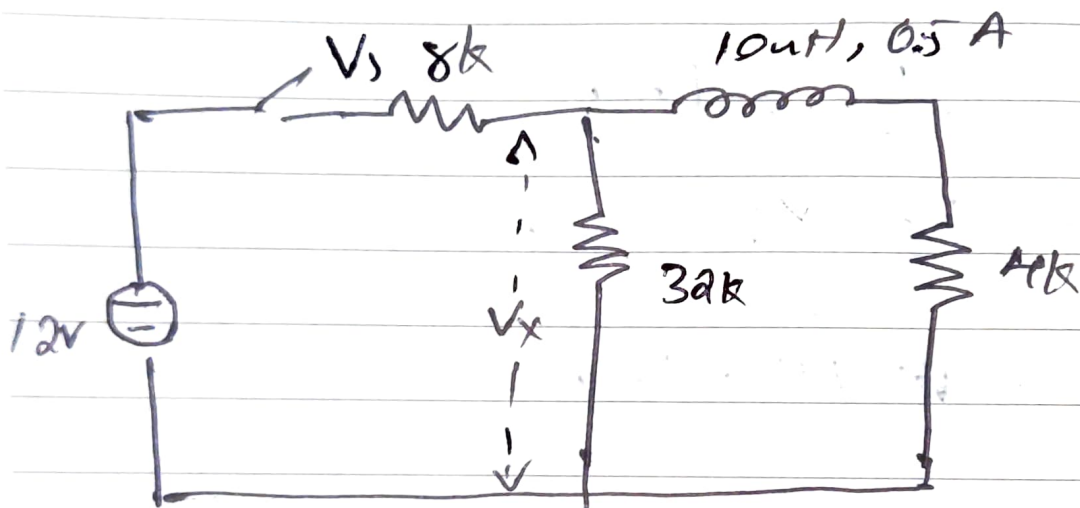

Find V_x @

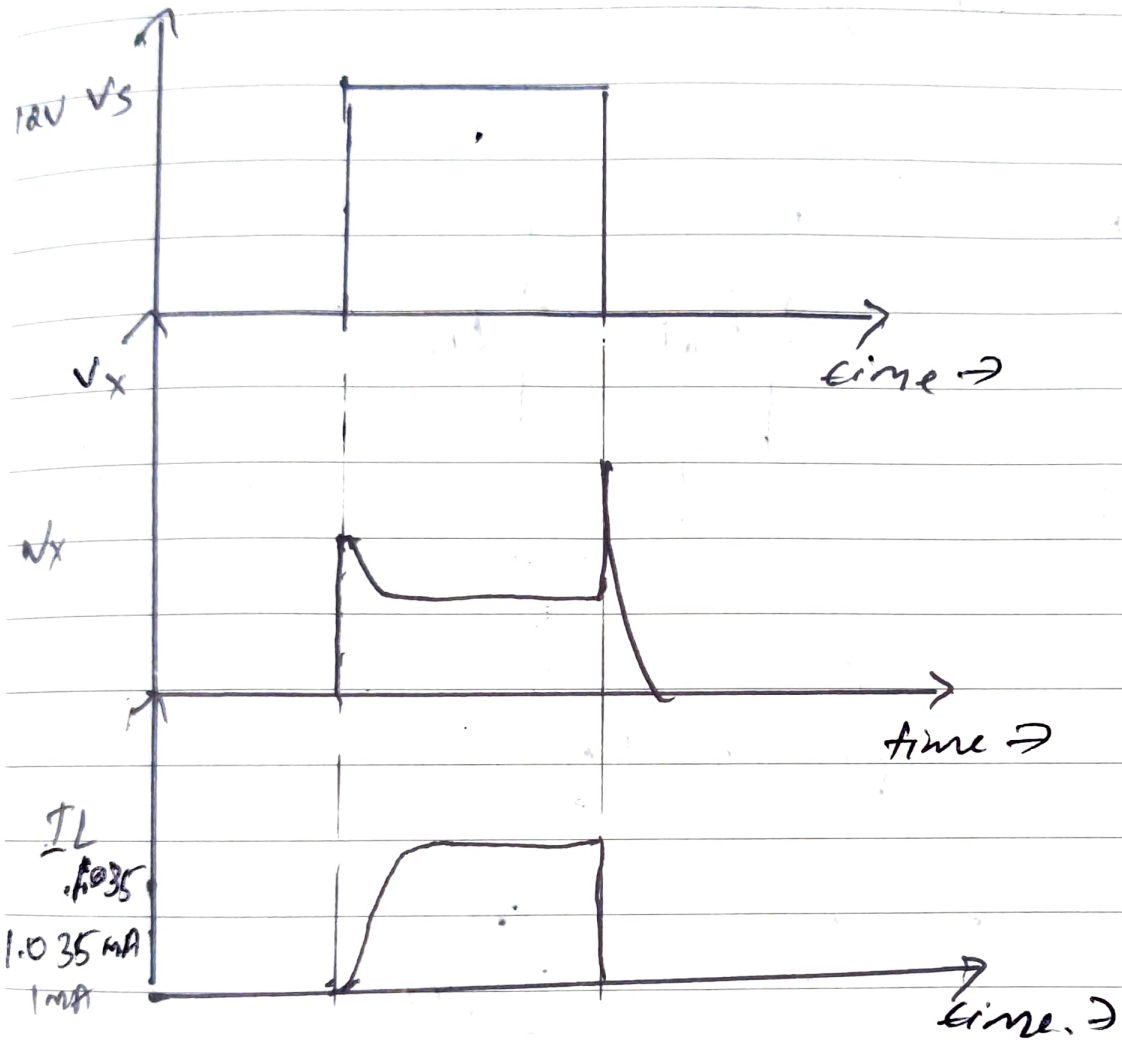- Instant of closing the switch S_1
- Steady state after closing the switch S_1
- Instant of opening the switch S_1



• Instant of closing S_2


$$V_X = V_S \times \frac{32k}{32k + 8k} = \frac{12 \times 32}{40} = 9.6V$$

$$I_S = \frac{V_S}{(32k + 8k)} = \frac{12}{40} = 0.3 \text{ mA}$$

$$\therefore V_X = 9.6V$$

Date: _____

• At steady state

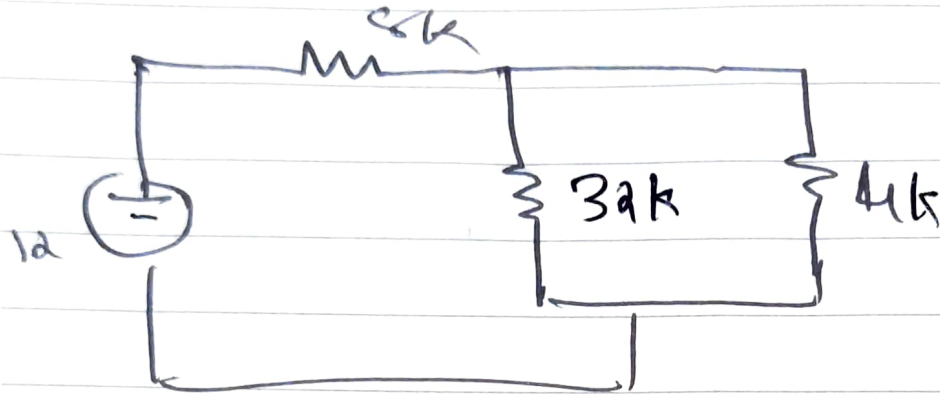


$$I_s = \frac{12}{8k (32k \parallel 4k)}$$

$$32 \parallel 4k \Rightarrow \frac{36}{32 \times 4}$$

$$\approx 3555.55 \Omega$$

$$= 3.55 k\Omega$$

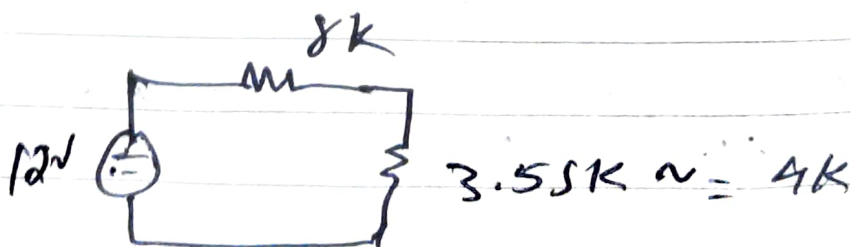

$$I = 1 \text{ mA}$$

$$V_x = 3.55 \times 1\text{mA}$$

$$\text{or } \approx 4000 \times 1\text{mA}$$

$$\approx \underline{\underline{4\text{V}}}$$

$$\text{or } 3.692\text{V} //$$

• When switch closed.

$$I = 0$$

$$V = \frac{E}{t}$$